




# Lab 7 Preparation




# Lab 7 Components

- **Part I:** Create a memory unit
  - **Part II:** Interface with the RGB Video
  - **Part III:** RGB Video animation (bonus)
- 
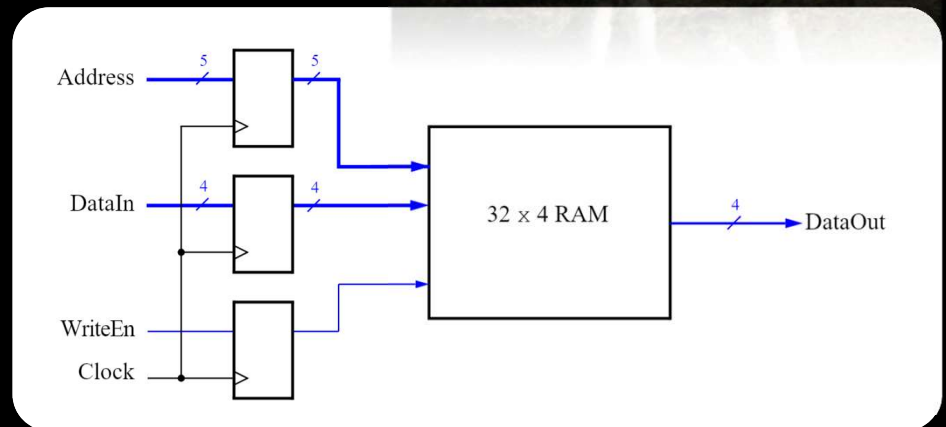
# Part I: Memory Unit


- Creating a mini-RAM unit.
- Make use of the built-in **RAM**
  - Follow lab instructions to create a 4-bit RAM unit with 32 words.
  - Fill the RAM with values 0-F.
- Once completed, connect this RAM to the HEX display.


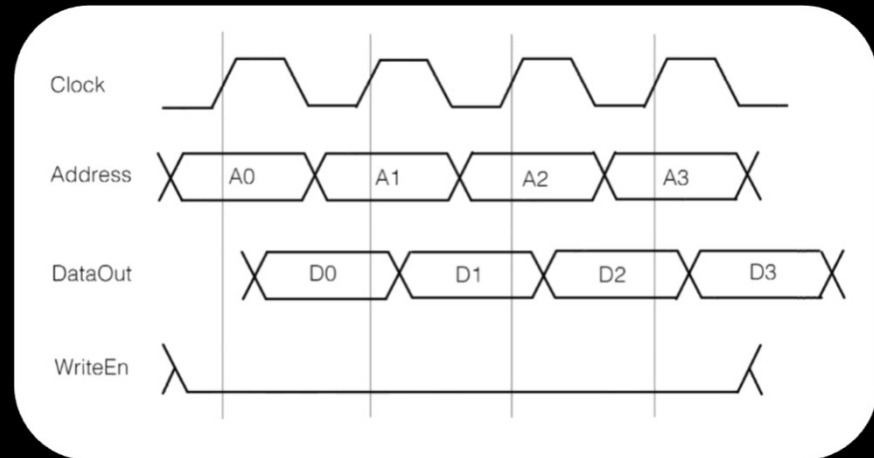
# Part I: Read & Write Timing


- **Read:**

- Note slight delay after clock signal, before data appears.




- **Write:**

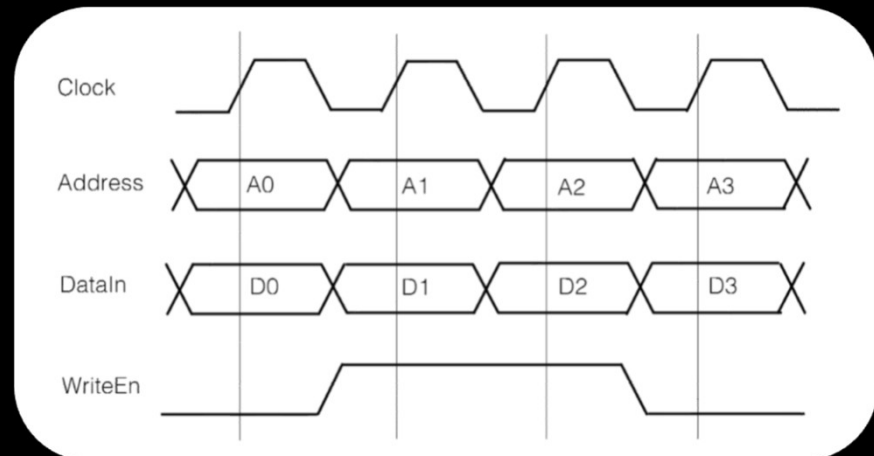- Note that only D1 and D2 are written (because of the WriteEn signal).



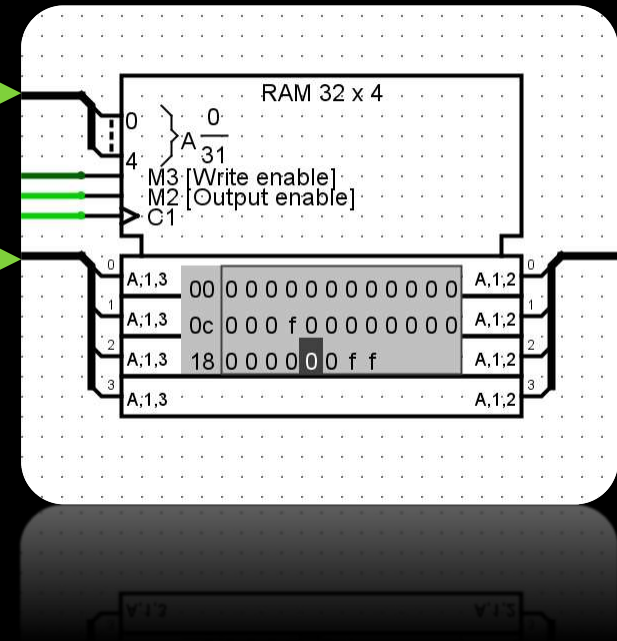
# Part I: Filling memory

- Connect address register and data register to RAM.
- Fill all RAM locations with increasing values, starting at 0 at address 00000.
- Connect output to 7-segment display.



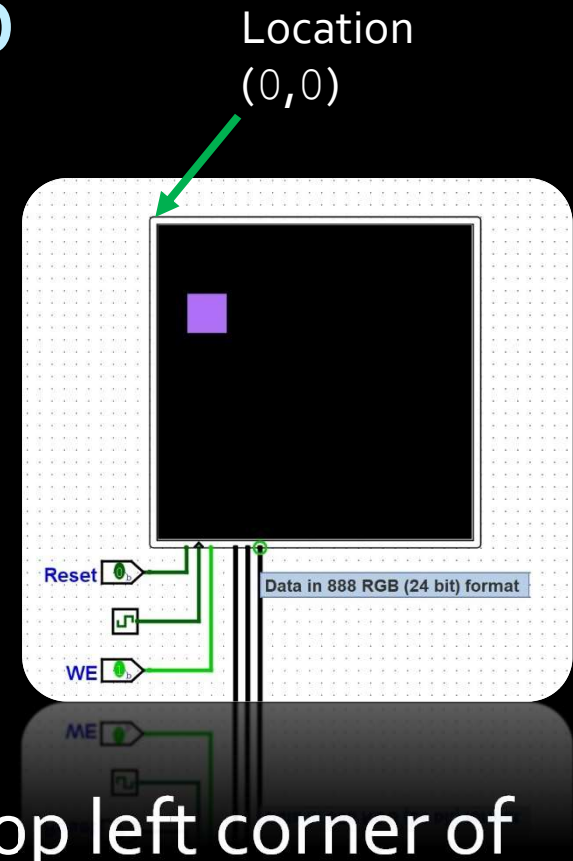
## Part II: RGB Video

- The RGB Video component models the VGA display in the lab workstations.
- For this part, given input coordinates  $X$  and  $Y$ , draw a  $16 \times 16$  box of coloured pixels, using  $X$  and  $Y$  as the top left corner of the box.



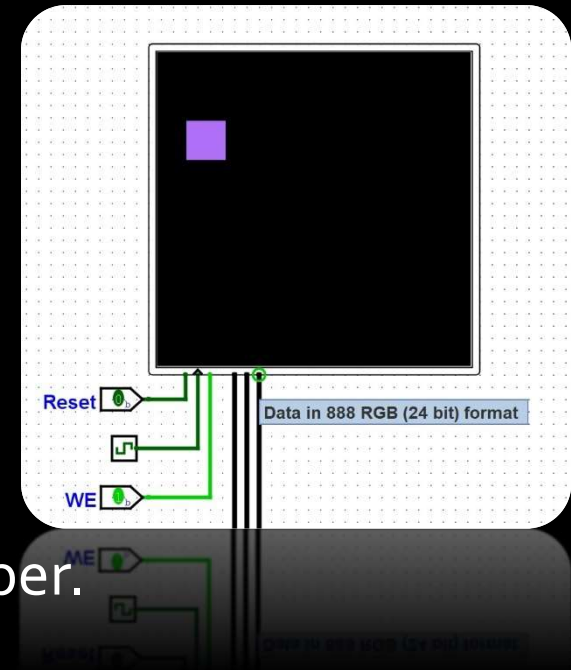
# Part II: RGB Video

- The RGB Video component has 6 inputs:
  - **Reset**
  - **Clock**
  - **Write Enable**
    - Like lifting/dropping pen on paper.
  - **X Coordinate**
  - **Y Coordinate**
  - **Data in 888 RGB (24 bit) format**
    - Three sections of 8 bits, representing the RGB values for the pixel (see next slide for more detail)


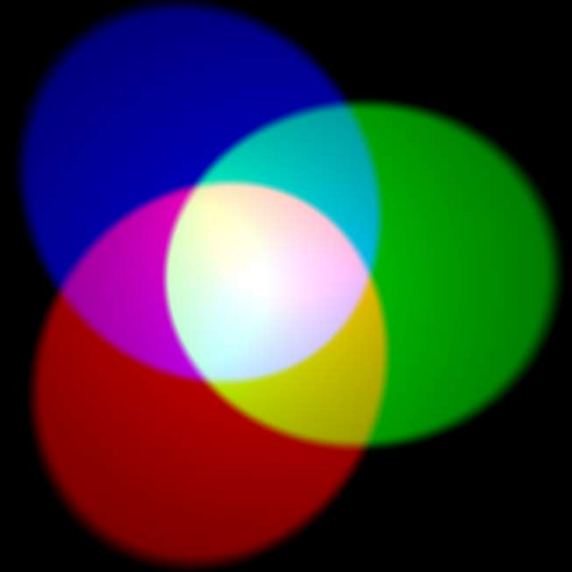
# Part II: RGB Video

- Light colours are additive.
  - As opposed to paint, which is subtractive.
  - Light is made of red, green and blue components.
    - White light is the combination of all three.
- To create a colour, set the 8-bit values for the red, green and blue components and concatenate them into a 24-bit value.
  - Black = 0x000000, White = 0xFFFFFFFF





# Part II: RGB Video

- Circuit components needed:
  - **RGB Video**
    - built into Logisim, check the handout for input details
  - **Datapath**
    - Takes in:
      - $X$  and  $Y$  (through switches)
      - control signals (reset, clock, enable etc.)
  - **FSM:**
    - Controls datapath to load  $X$  and  $Y$  values, and iterate through the pixel locations that need to be updated (relative to  $X$  and  $Y$ ).

# Part II: RGB Video

- Hints:

- Have tests to verify that each component works on its own.
  - Try using the RGB Video to draw a single pixel,
  - Make sure the datapath works on its own,
  - Verify the state transitions of the FSM.
- Consider using counters to store the offsets from  $X$  and  $Y$  that need to be displayed.

- **It's Lab 7.** You have full freedom to implement this however you like 😊

## Part III: Animation (bonus)

- Note: This part is optional, but can be done for bonus marks in the course.
- Animate a box by drawing it, then waiting, then drawing another at a different location, then waiting...
- Many projects will use animation in some form, so you should try this part out!
  - Also...bonus marks! 😊

