

Course: CSC258F

Professor: Steve Engels

Experimenter: Yuhao Yang

Student ID: 1005808057


# Lab4

## Pre-Lab Report

## Part1:

1. Build the D latch and master slave flip-flop in Logisim in different modules.

### *D latch circuit*

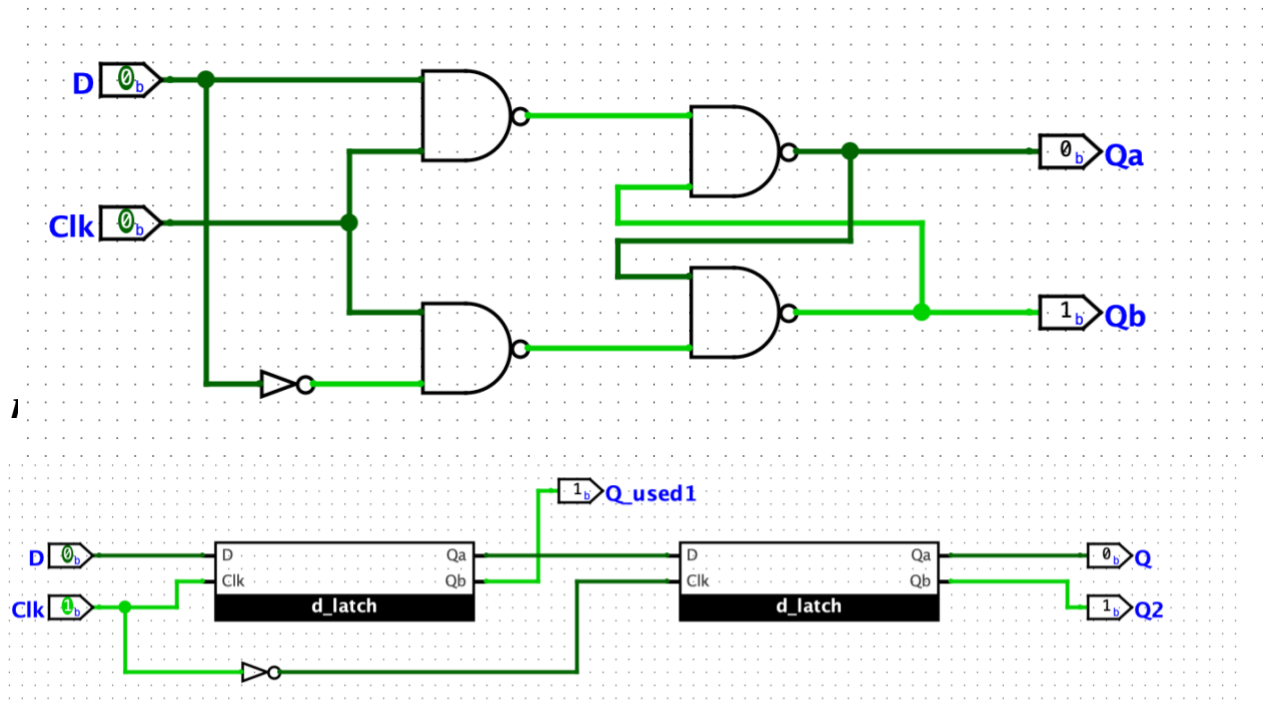

2. Show the circuit is correct by using Poke.

*Showed on Logisim.*


3. For the D latch and the flip flop, are there any input combinations of Clk and D that should NOT be the first you test?

*From my perspective, all combinations for the D latch should not be the first test, because no matter Clk takes value of zero or one for the first test, one of the D latches will have zero as input of Clk since inverter. As we know, when Clk is zero, then the D latch will keep the previous state, but there is no previous state for both D latches when I first test, then it will raise an error. Same to flip flop, one of D latch*

*will have zero of Clk, but there is no previous state for that D latch, so the flip flop will raise an error for all combinations of Clk and D.*

## Part2:

### 1. Build the circuit in Logisim.

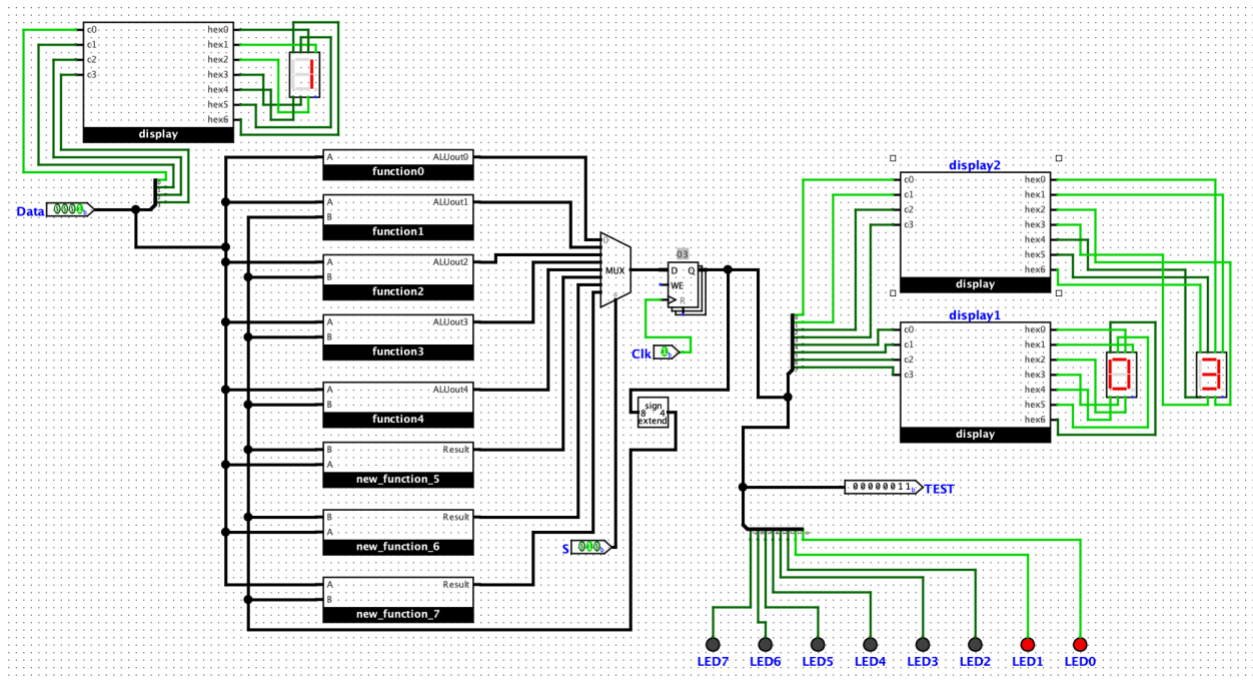

2.

a) What would happen if we remove register in the circuit?

*By observing the circuit, we know that if we remove the register, then the function 1 to function 7 will not have input signal B, and it will cause errors if we select function 1 to 7 in MUX.*

b) How many bits we need to store the result if we multiple two n-bit binary number?

*If we multiple two n-bit binary number, then we need  $2n$  bits to store the result.*

3. Answer the questions below.

a) Let data to be zero than we set clk to be one, then set clk to be zero and change s to be 001 from 000 which means we changed to the next function and set clk to be one again, we just need to follow this process and we can get a correct and net sequence.

Data	Function	S	A	B	clk	TEST
0001	0	000	0001	X X	1 0	0000001
0001	1	001	0001	0010 0011	1 0	00001111
0001	2	010	0001	0011 0100	1 0	00000100
0001	3	011	0001	0100 0101	1 0	01001010
0001	4	100	0001	0101 0101	1 0	00000001
0001	5	101	0001	0001 0001	1 0	00000010
0001	6	110	0001	0001 0001	1 0	00000001
0001	7	111	0001	0001 0001	1 0	00000001

The order from top to bottom


b) Use test vector to show new operations are correct.

## Function5


The image shows a Logisim circuit diagram at the top and a test vector window below it. The circuit diagram shows two 4-bit registers, A and B, connected to a 4-bit adder. Register A is initialized to 0000 and Register B is initialized to 0000. The adder's output is connected to a 4-bit display labeled 'Result'. The test vector window is titled 'Logisim: Test Vector new\_function\_5 of part2' and shows a table of test cases. The table has columns for 'status', 'A', 'B', and 'Result'. The test cases are as follows:

status	A	B	Result
0000	1011	0000	1011
0001	1011	0001	0110
0111	1011	1000	0000
0100	0101	0101	0000
1000	1011	0000	0000
1001	1011	0000	0000
1111	1011	0000	0000

At the bottom of the window, there are buttons for 'Load Vector', 'Run', 'Stop', 'Reset', and 'Close Window'.

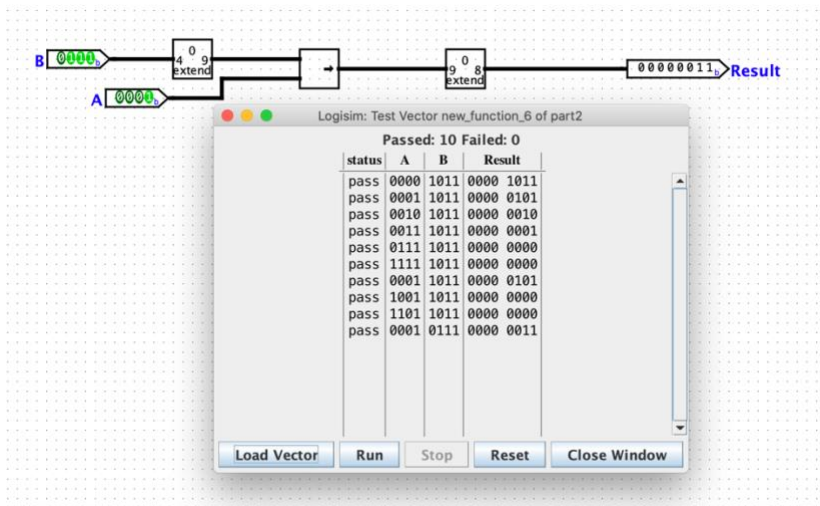**Function6**

### Function7

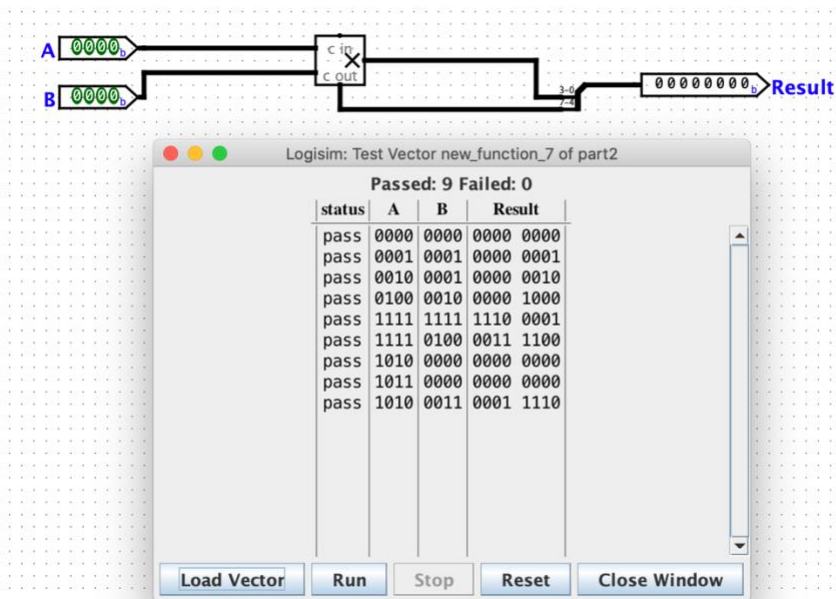


## Part3:

1. What is the behaviour of the 8-bit shift register shown in Figure 5 when Load  $n = 1$  and ShiftRight = 0?

***When Load  $n = 1$  and ShiftRight = 0, the output will remain the previous state because load\_val cannot pass the second MUX in ShiftBit.***

2. Draw the schematic

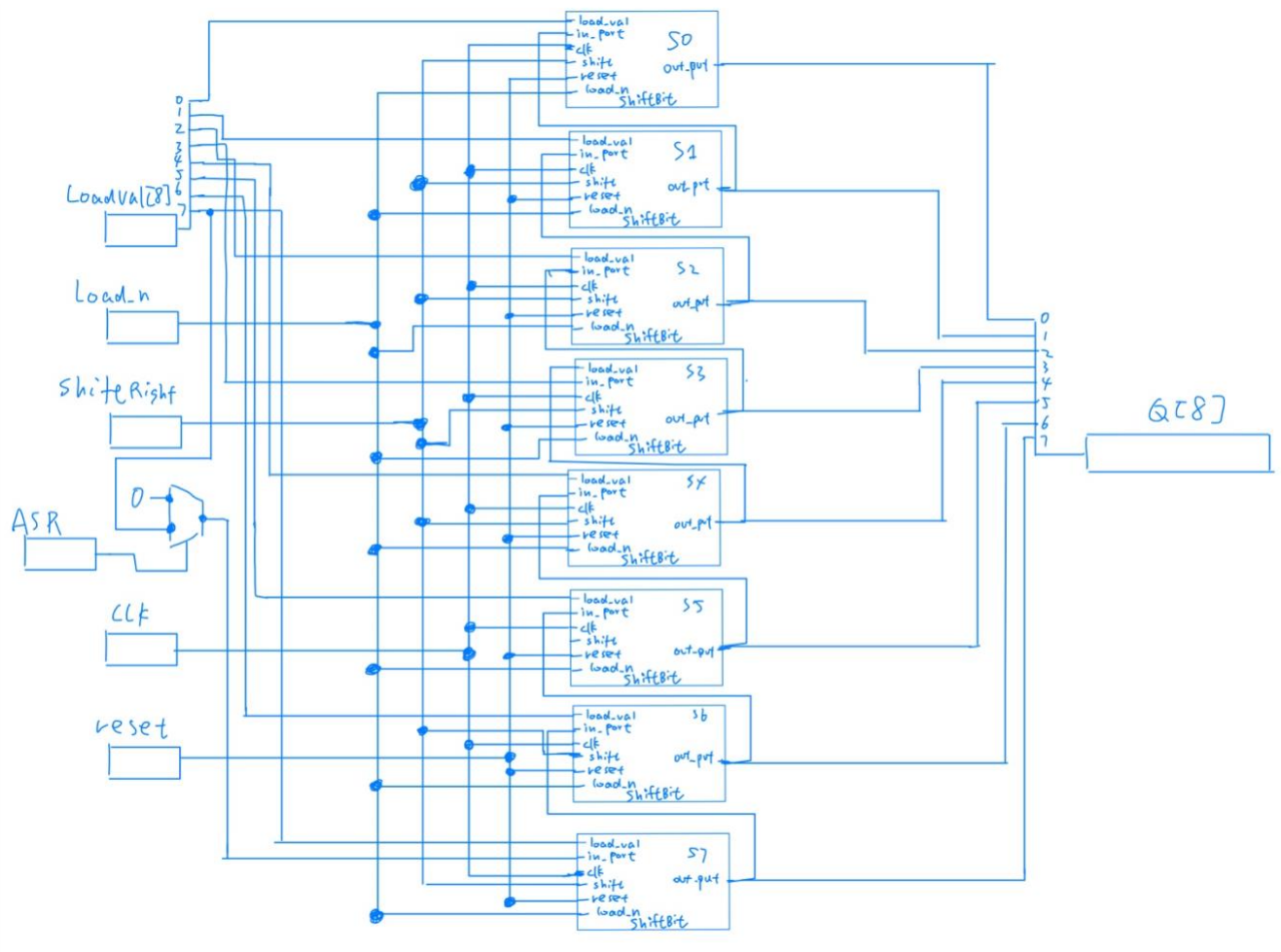

4. Show the circuit in Logisim.

