




Lab 1 – Preparation



Today's Tutorial

- Learning objectives for Lab 1
- Lab 1 parts
 - Warm-up exercise
 - What to hand in
- Intro to Logisim

Learning objectives

 


Lab 1 Learning Objectives

- What are the labs about?
 - Creating demo-worthy designs.
- What is Lab 1 about?
 - Learn how to build logic circuits by using logic gates.
 - Produce truth tables for a given design (starting either from a given logic function or from a description of the design's behaviour).
 - Demonstrate familiarity with the graphic tool Logisim.


Approach to Lab 1

- Experience is the best teacher.

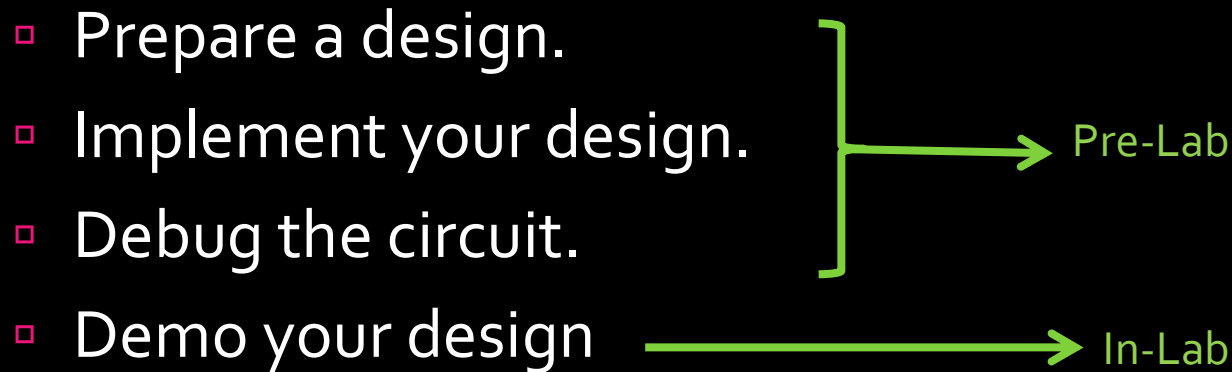

- Try to think of your prelabs as “an assignment due before the beginning of the lab”.


Lab Breakdown

 

Lab 1 breakdown

- Mark breakdown:
 - Pre-lab: 2 marks
 - Part I: 2 marks
 - Part II: 2 marks
 - Part III: 2 marks
- Part I:
 - Design circuit for multiplexer:

$$F = X\bar{S} + YS$$

 

Lab 1 breakdown

- Part I (cont'd):
 - Note that the following are all different ways of expressing the same thing:
 - $F = X\bar{S} + YS$
 - $F = X * S' + Y * S$
 - $F = (X \text{ and (not } S)) \text{ or } (Y \text{ and } S)$
 - Need to represent this logical expression in gates.
 - Need to show the truth table for the three inputs X, Y & S and the output F .
- Part I doesn't involve Logisim yet 😊

Lab 1 breakdown

- Part II:

- Given the function:

$$f = (a+b)' + cb'$$

- How would you implement this in gates?
 - What is the minimal number of gates you need?

- Part III:

- Implement these circuits in Logisim.
 - Test your designs (using Poke tool and test files)

Warm Up Example

- Design a circuit that implements the following logic function, using only 2-input AND and 2-input OR gates.

$$f = a * b + (c + b)$$


- Write down the truth table for this design.
 - Note: This expression is common shorthand for:

$$f = a \text{ AND } b \text{ OR } (c \text{ OR } b)$$

Warm Up Example cont'd

- Is there a cheaper implementation (i.e., with fewer gates)?

- $f = a * b + (c + b)$

 

What to hand in



Prelab vs Lab Demo

- Prelab exercises are due before 6pm on lab days.
 - Written/hand-drawn elements in PDF files.
 - Logisim circuits as *.circ files.
 - Logisim tests as *.txt files.
- TAs will definitely ask to look at your Logisim designs, so be ready to share your screen with them.
 - Also be ready to share the hand-written elements in case a question arises about your design process.


Pre-lab reports

- The hand-written report should include the following:
 - Lab number and title
 - Student info (last name, first name, student #)
 - Exercise parts
 - Each in its own clearly-labeled section.
 - Restate the question (summarized).
 - Provide the calculations (if applicable).
 - Illustrate the solution (including pin labels).
 - PLEASE BE NEAT.
- The Logisim files should be named to reflect the lab number and part number.
 - e.g. `lab1_part2.circ`

Things to note

- This will be the easiest lab you do in the course.
- Whenever possible, use the tools and submit a printed pre-lab report.
- Try to come up with the smallest circuits possible.
 - How do you reduce a complex circuit?
 - For now, think back to boolean algebra axioms!
 - Simple reasoning helps as well 😊

Intro to Logisim

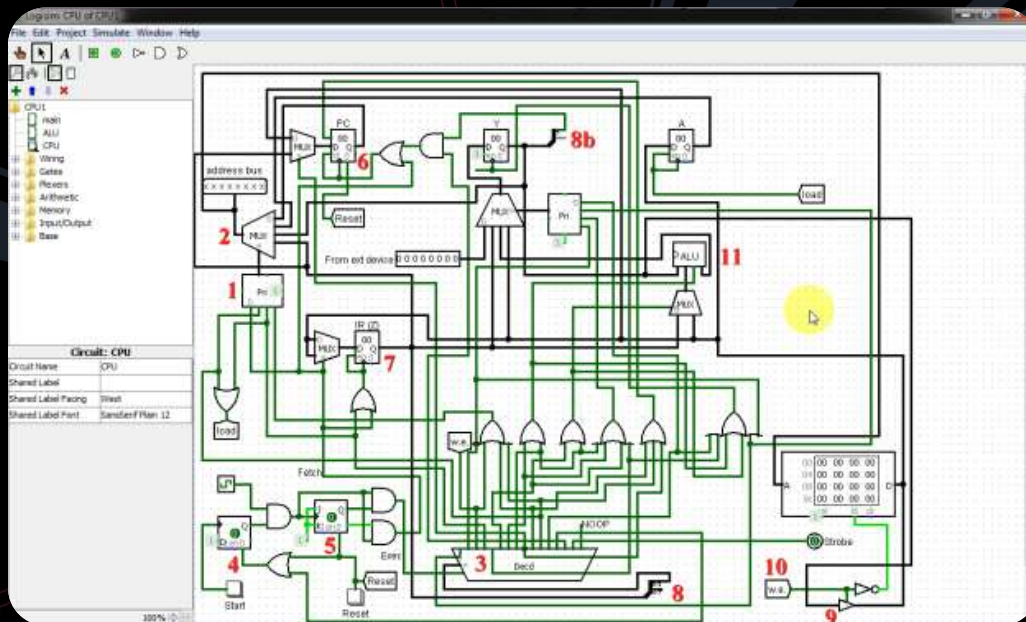

Logisim installation

- Logisim is a powerful logic circuit simulation environment.
 - In this course, we will be using version 3.3.0
 - <https://github.com/reds-heig/logisim-evolution/releases/tag/v3.3.0>
 - Just the `jar` file is needed.
- Note:
 - Make sure to use Logisim-Evolution downloaded at the above link. Do NOT use the original Logisim or any other variations or versions of it.
 - You will need Java 13 installed to launch this.

Logisim walkthrough

The screenshot displays the Logisim software interface with four main panels highlighted by red boxes:

- Components:** A tree view on the left showing a hierarchy of components including main, Wiring, Gates, Plexers, Arithmetic, Memory, Input/Output, TTL, TCL, BFH mega functions, Input/Output-Extra, and System On Chip components.
- Tools:** A toolbar at the top right containing various icons for drawing and editing logic components.
- Properties:** A panel at the bottom left showing the properties of the selected component (Pin "c"). It includes tabs for VHDL and Verilog, and a table of properties.
- Canvas:** The central workspace where a logic circuit is being built. It shows two input pins labeled 'a' and 'b' connected to an AND gate, which is then connected to an output pin labeled 'c'.

The Properties panel for Pin "c" is detailed below:

Selection: Pin "c"	
VHDL	Verilog
Facing	West
Output?	Yes
Data Bits	1
Three-state?	No
Pull Behavior	Unchanged
Label	c

At the bottom of the Properties panel, there is a section for "Zoom and grid control:" with a zoom level of 100% and an "Auto" button.

Tools/Views



Poke: Click on wires to inspect their state, click on most components to change their state.

Tools/Views



Select: Selects and moves things in the canvas, and manipulates wires/buses. Click and drag from inputs/outputs to create wires/buses.

Tools/Views



Wire: Creates wires on the canvas.

1111



Text: Add text on the Canvas.

Tools/Views



Default Input/Output: default type of input and output for the circuits. You will be using them a lot throughout the course.


Tools/Views



Logic gates: some commonly used logic gates that you can click and drop on the canvas to build your circuits.


Canvas

 - Canvas is where you will be building your circuits by dropping components on the canvas and then connect them with wires.




Wires

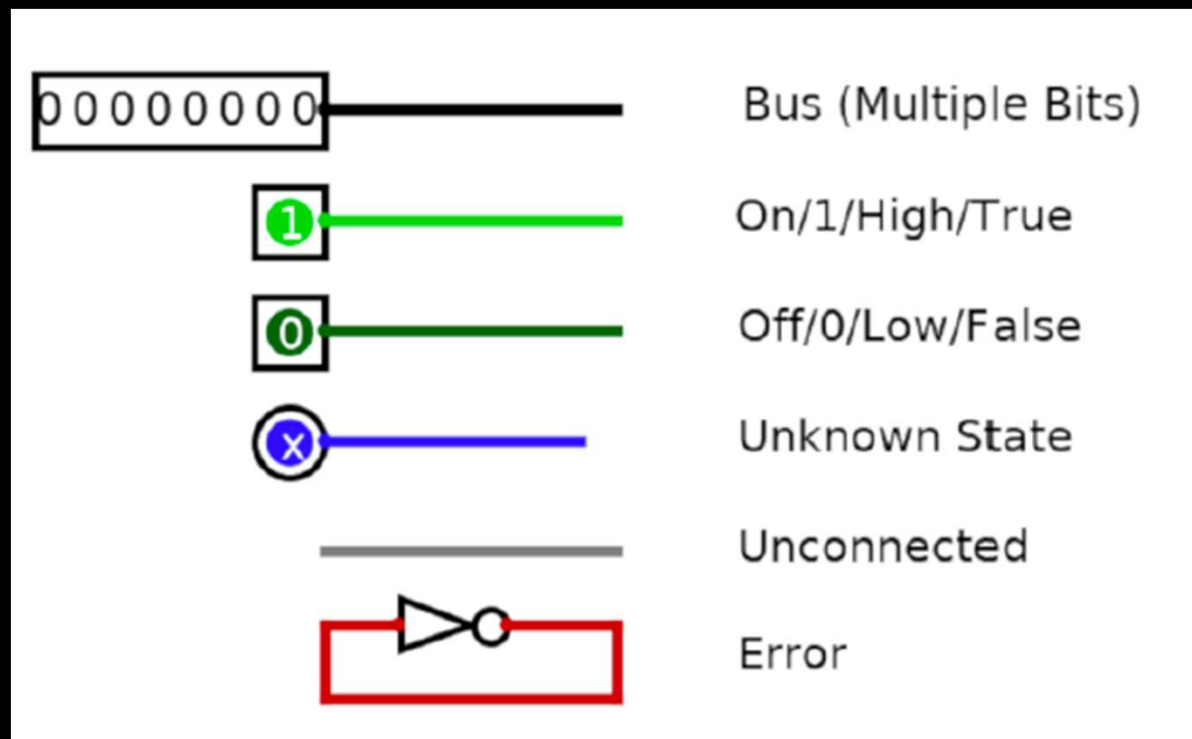- Wires and buses can have many states. You can inspect the state of a wire/bus using **poke** in the toolbar.



Components

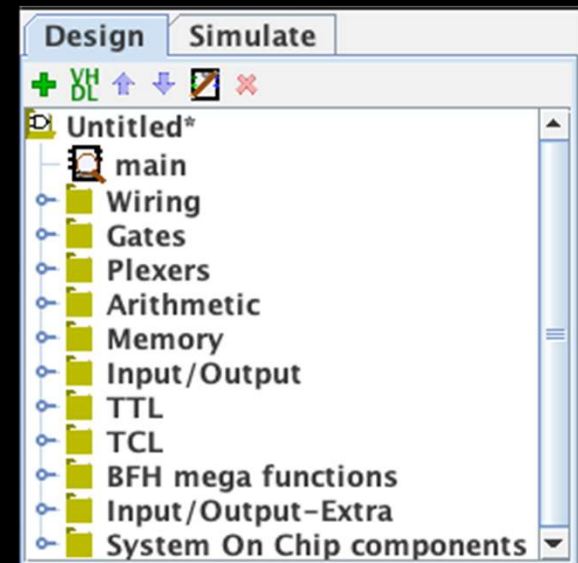- This contains all the circuits in this le as well as all the built-in components.
- Double-click on each circuit to view it. To place a component from this list, select it, and then click somewhere in the canvas.
- You can add/delete a circuit using the green + sign and the red x sign on the top.







Properties

- If you click on a component on the canvas, you would be able to view and edit its properties.
- For example, this is the properties for an AND gate. You can change the number of input bits and number of inputs here. This will be useful in the future.

Properties		State
Selection: AND Gate		
VHDL		Verilog
Facing	East	
Data Bits	1	
Gate Size	Medium	
Number Of Inputs	2	
Output Value	0/1	
Label		

Testing in Logisim

    - The easiest and most visual way of testing is using the Poke in the tool bar and click on the components to change the state. This will be very useful throughout the course so make sure you try this out.



Testing in Logisim

- Another way is through test vector files.
(details can be found in the lab handout)
- Steps involved:
 1. list the truth table for your circuit, the values for the inputs and the expected values for the outputs
 2. Logisim will be able to run the tests according to your truth table to test the functionality of your circuit.