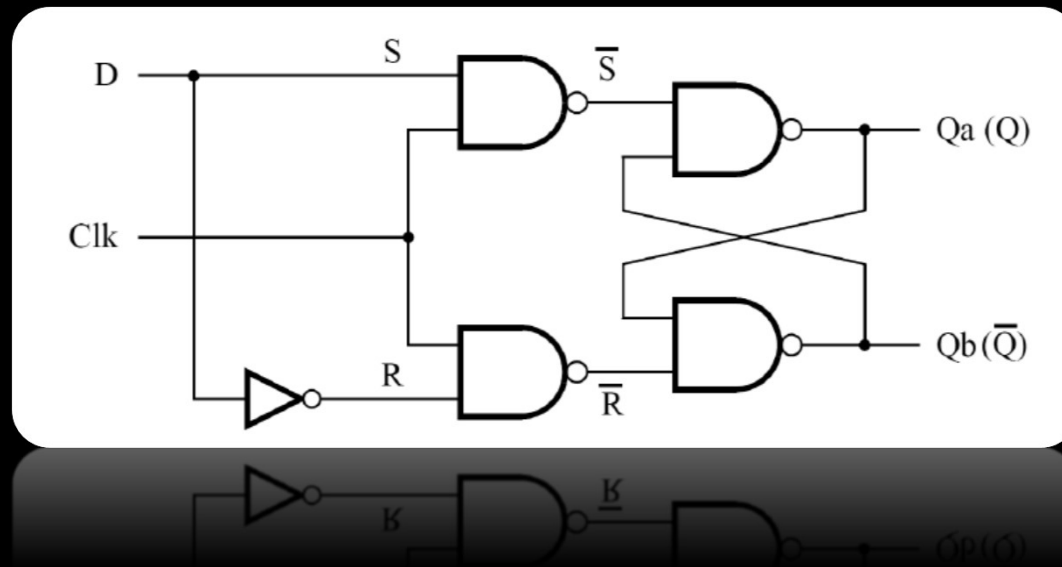




Lab 4 Preparation


Lab 4 – Part I

- Create a D latch out of NAND gates.




Lab 4 – Part I

- Then, create a D flip-flop out of D latches.

 


Lab 4 – Part II

- Enhance the ALU from last week:
 - More operations (e.g. multiplication, shifting)
 - Memory (aka registers)

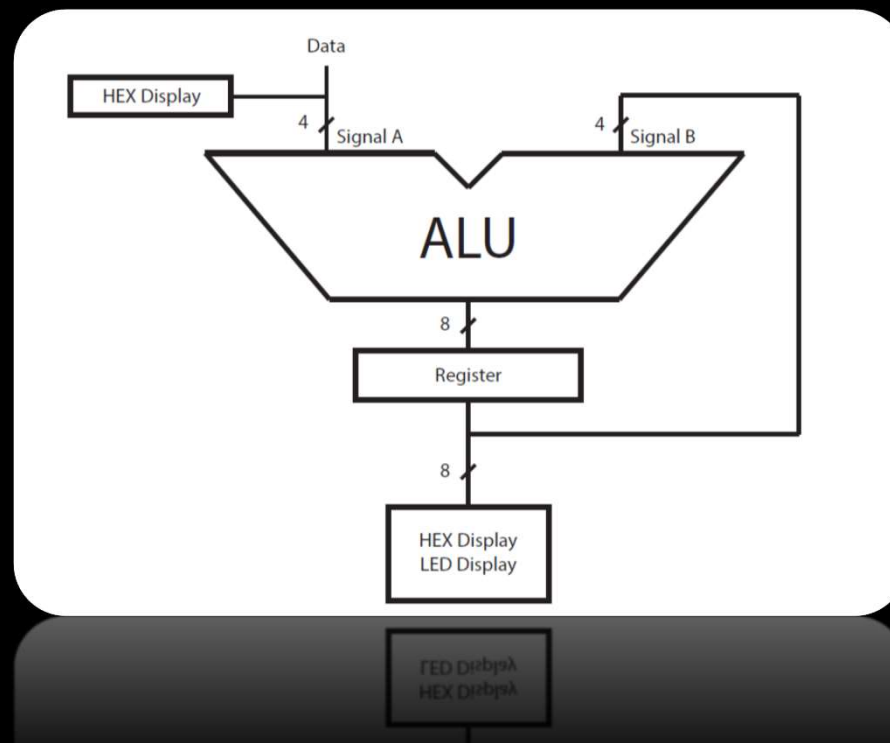

Lab 4 – Part II

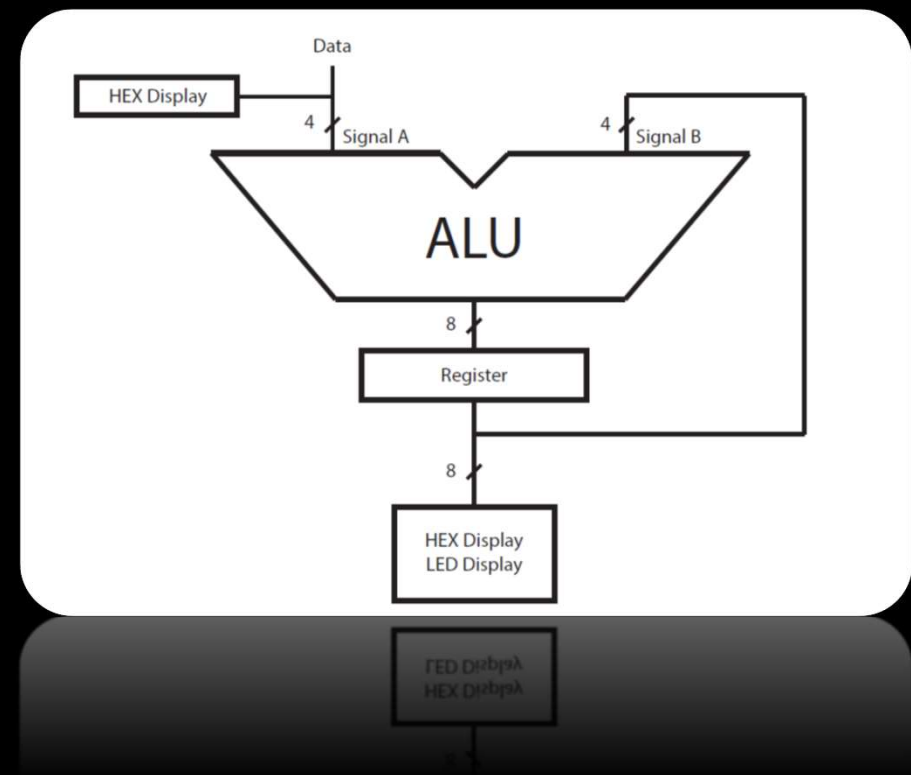- New operations:
 - Left shift
 - Logical right shift
 - Multiplication
- All of these are supplied through the collection of components in Logisim.





Logic vs. Arithmetic Shift

- Arithmetic right shifts **replicate the sign bit** instead of using zero to fill in the most-significant bit(s).
 - Needed if dealing with signed numbers (e.g., 2's complement notation)
- Logical right shifts fill in missing bits with zeroes.
- Example: Shift 10010000 right by 3 bits
 - Arithmetic → **111**10010
 - Logical → **000**10010


Shifter Components

- Can be found under Arithmetic > Shifter.
 - You can change the shift type in Properties.
 - More details can be found at:
 - <http://www.cburch.com/logisim/docs/2.3.0/libs/arith/shifter.html>
- Logic Shift (left or right)

  


Lab 4 – Part II

- Note: ALU output is now stored in a set of flip-flops called a **register**.
 - 8 bits (flip-flops) long
 - Component found in Memory > Register.
 - You can change the Number of flip-flops in Properties > Data bits.

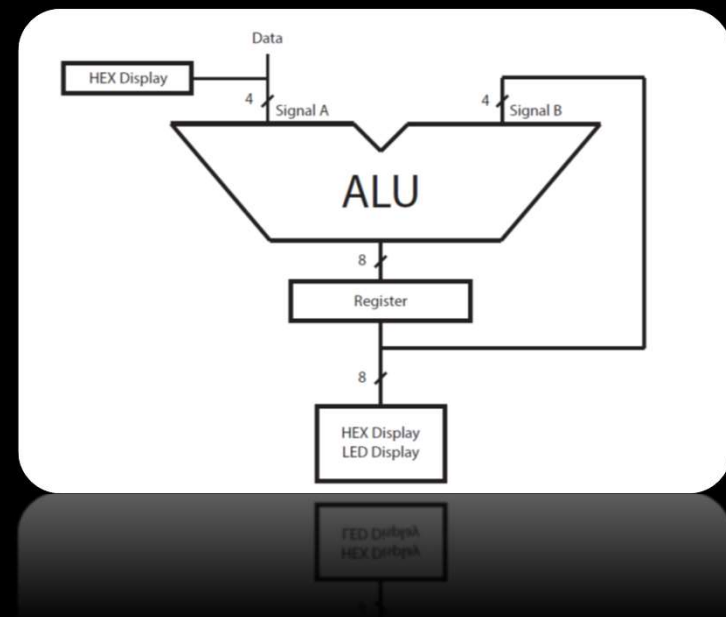


Lab 4 – Part III

- Make a shifter unit, for a single bit.
 - ▣ See diagram below.

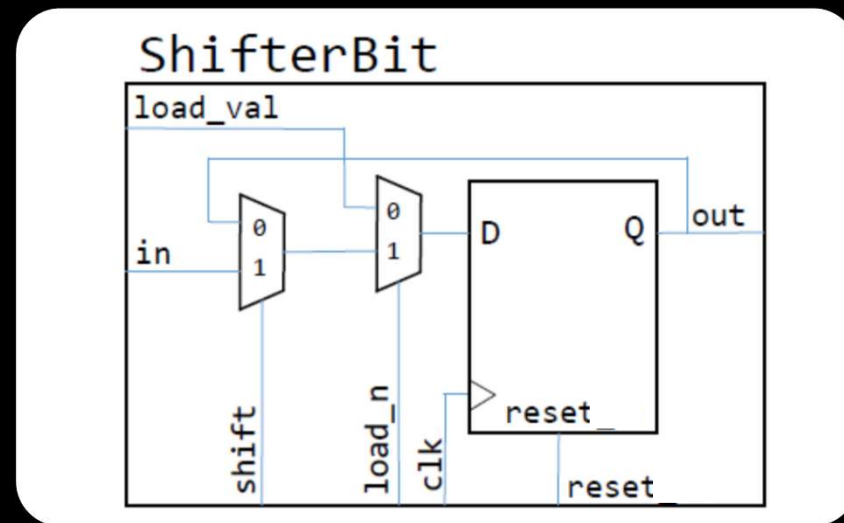

Lab 4 – Part III

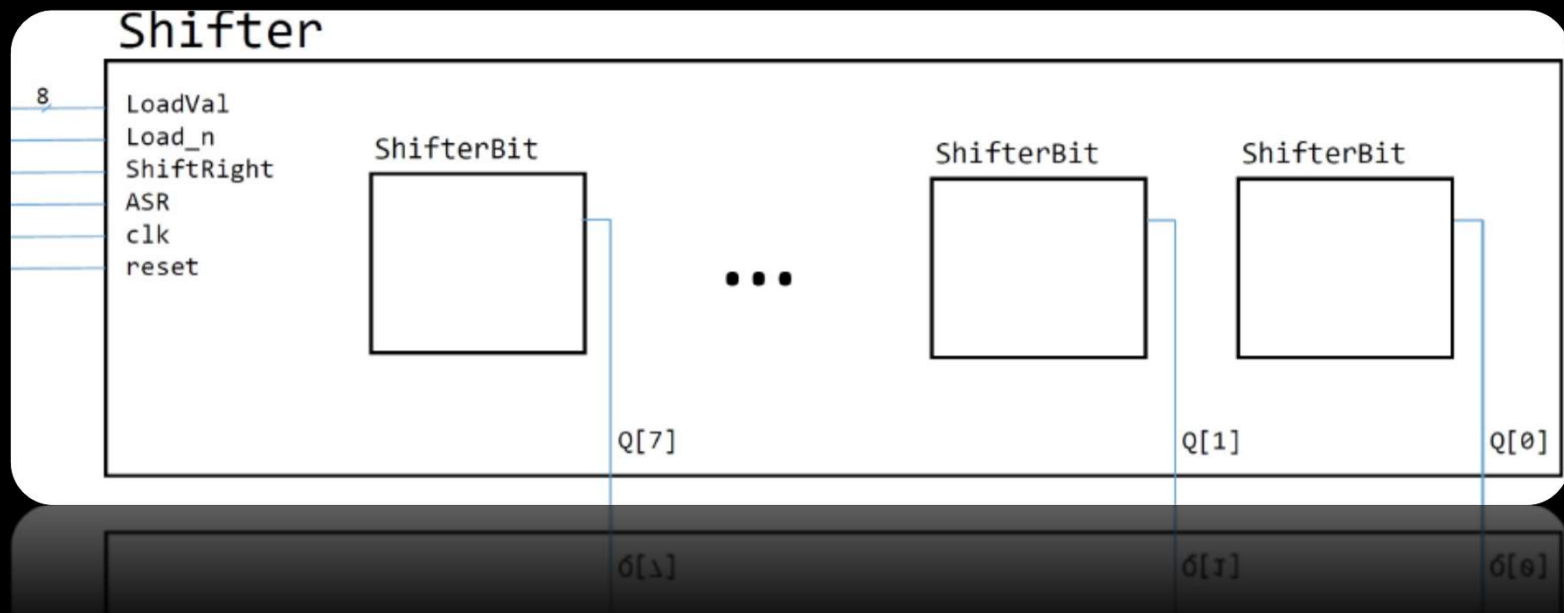- Connect 8 shifter units together.
- Note:
 - `Load_n` is active-low, loads all bits from `LoadVal` into `ShifterBit` units when `clk` goes high.
 - `reset` is asynchronous (doesn't wait for `clk` signal).
 - `ShiftRight` tells you when to shift, `ASR` tells you what kind of shift to do.



Why is Shift Important?

- What is the sum of 01101101 and 01101101?

11011010

Remember what happens here!

- Try the following:
 - 00110 logic shift right by 1 bit
 - 00110 logic shift left by 1 bit

A logic shift right of A by N bits results in: $A * 2^N$

A shift left of A by N bits results in: $A / 2^N$

Load register

- N-bit number = N D-flipflops synchronized to the same clock signal
- You can load a register's value (all bits at once), by feeding signals into each flip-flop:
 - In this example: a 4-bit **load register**.

