 




# Lab 2 Preparation


# Lab 2

- Lab 2 topics:
  - Multiplexers (cont'd)
  - Design hierarchy
  - Decoders
    - 7-segment displays
- The DE1-SoC
  - Connecting Logisim to DE1-Soc
- Intro to useful components in Logisim.


 
# Tasks for Lab 2


- Part I: Creating modules
  - Once created, a module can be used as a component.



# Tasks for Lab 2

- Part I: Creating modules
  - Create a simple module that makes a wrapper for the mux circuit we provide.
  - Set inputs to buttons (labeled SW0, SW1, SW2) and output to LED (labeled LEDR)
    - Labels correspond to DE1-SOC inputs and outputs

# Meet the DE1-SoC board!

 


# Meet the DE1-SoC board!

- In a non-COVID semester, we would be using Logisim to upload your designs onto the DE1-SOC.
  - Maybe in 2021 ☹
- What is the DE1-SOC?
  - It's a System On a Chip (SoC) with:
    - Altera's Cyclone® V 5CSEMA5F31 FPGA, and
    - a Dual-core ARM Cortex-A9 hard processor (HPS)
  - 64 MB SDRAM on FPGA device
  - Six 7-segment displays
  - 10 toggle switches
  - 10 LEDs
  - 9 green LEDs
  - Four pushbutton switches
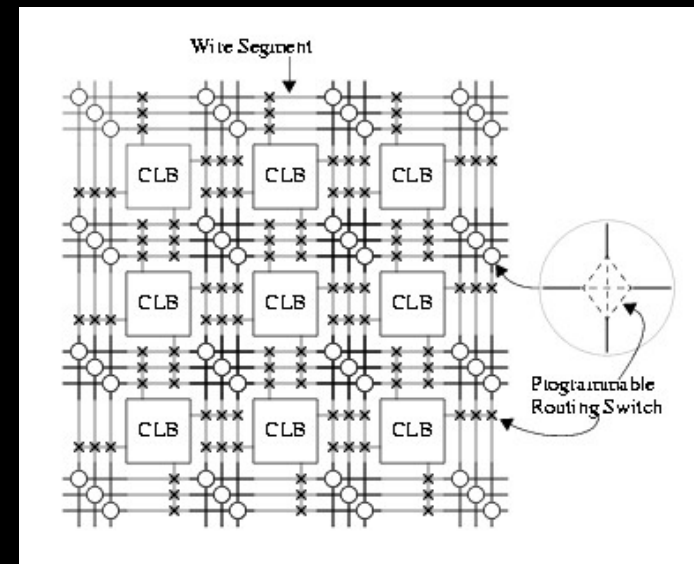
# What does that mean?

- Key term: **FPGA**.
  - Stands for Field Programmable Gate Array.
  - A regular network of logic that can be programmed and reprogrammed to implement any circuit.
  - Circuits aren't generally built by hand; they're programmed using languages like Verilog, VHDL or Logisim.



# Connecting Logisim to DE1-SoC

- The circuits we build in Logisim can be downloaded to the DE1-SoC board.
- You can map your inputs/outputs in Logisim to the switches or LEDs on the DE1-SoC board and then test your circuit on the board.
- Even though we currently do not access to the boards in the lab, it is still good to know the process and learn about the board.




# Connecting Logisim to DE1-SoC

- The details about the process can be found in lab2 handout.
- If you want to upload your design:
  - Make sure that you follow the steps carefully and understand how the circuit would have been if it can be downloaded on the board.
  - Note: you will need a tool called Quartus installed to compile in Logisim. Therefore we encourage you to test out the compilation of your design on the teach.cs machines. Quartus has been installed on them.



# Tasks for Lab 2

- Part II: Designing with modules.

- Make a 4-to-1 mux out of 2-to-1 muxes.

 

$s_0$	Y
0	A
1	B

  


$s_1$	$s_0$	Y
0	0	U
0	1	V
1	0	W
1	1	X
 
# Tasks for Lab 2


- Part II: Designing with modules.
  - If each 2-to-1 mux can handle 2 inputs, how to build something that handles 4?
  - How would you make a 4-input function out of 2-input functions?

The select bits will be the trickiest part 😊



 
# Tasks for Lab 2

- Part III: The 7-segment decoder.
  - This is one of the components in the Logisim toolkit.
  - Also one of the components on the DE1-SOC board!



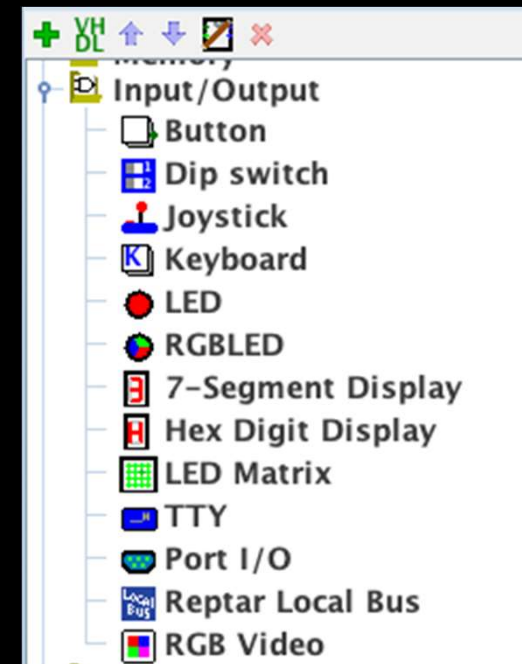
# Exploring Logisim Components

- This components and others are listed under Input/Output, for future reference:
  - Button: Can be mapped to the switches and buttons on the DE1 board. Only outputs a 1 when held down with Poke.
  - 7-Segment Display: Can be mapped to the 7-segment display on the DE1 board.
  - LED: Can be mapped to the outputs on the DE1 board.
- Note: always start with the default input/output type from the tool bar and only switch to the above if necessary



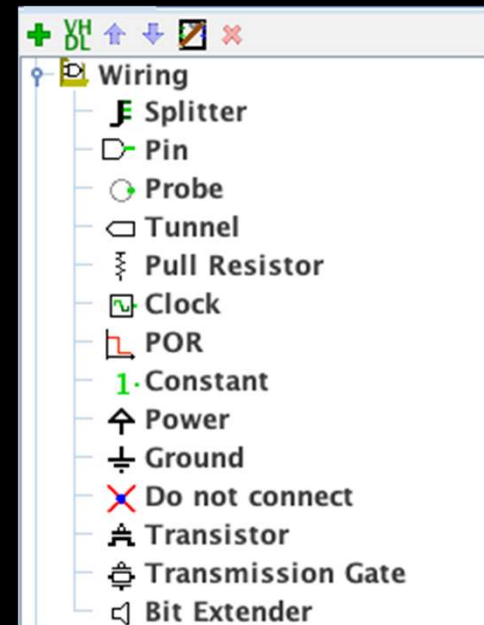
# Useful Components in Logisim

- Wiring:
  - Splitter: Splits buses into individual wires or smaller buses. Works both ways.
  - Clock
  - Constant: Outputs a constant value (can be multiple bits on a bus).
  - Bit Extender: Pads or sign extends bits on a bus.
- You can even make a transistor circuit with the components at the bottom 😊



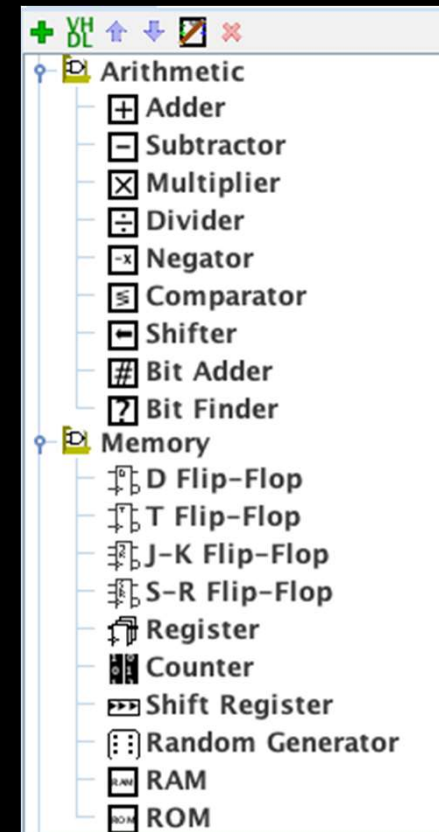
# Useful Components in Logisim

- Arithmetic and memory:
  - Some of the arithmetic components will be useful in later labs. Details about each one can be found in:  
<http://www.cburch.com/logisim/docs/2.3.0/libs/arith/index.html>
    - This doc is for an earlier version, some components may look different now.
  - We will be exploring the memory components later in the course.


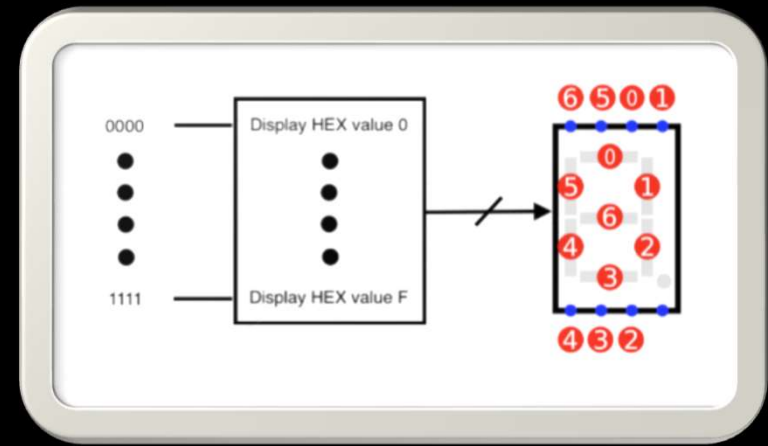
# Tasks for Lab 2

- The diagram on the right illustrates how to use the inputs to the 7-segment decoder (or the HEX decoder) to activate the segments.
- Each segment is **active-high**, meaning that if you set an input to 1, the corresponding segment will turn on.
  - The DE1-SOC board is the opposite (i.e. **active-low**)







# Tasks for Lab 2

- Ultimate goal:

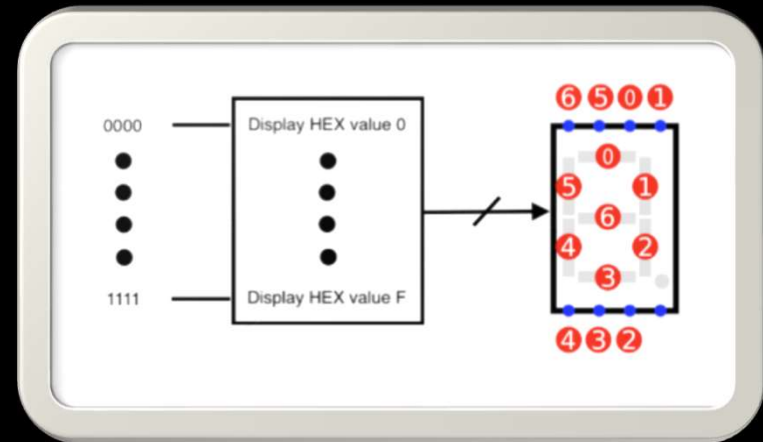 1. Take a 4-bit input coming from the switches on the and interpret those as binary number:




2. Create seven circuits, one for each segment on the right to activate each segment based on the 4-bit input values.
  - For example: If input is 0000, display "0" on the segments. If input is 1111, display "F" on the segments.

# Activating 7-seg displays

- The diagram on the right illustrates the 16 digits we want to show on the 7-segment display.
- How do we make this happen?
  - Consider segment 0 (the top segment in each digit).
  - Need to set it high in the following input cases:

<u>Input</u>		<u>Display</u>
0000	--	"0"
0010	--	"2"
0011	--	"3"
0101	--	"5"
0110	--	"6"
0111	--	"7"
1000	--	"8"
1001	--	"9"
1010	--	"A"
1100	--	"C"
1110	--	"E"
1111	--	"F"

 

- How do we express this?

# Activating 7-seg displays

- Answer: Karnaugh Maps!

	$\overline{SW1} * \overline{SW0}$	$\overline{SW1} * SW0$	$SW1 * SW0$	$SW1 * \overline{SW0}$
$\overline{SW3} * \overline{SW2}$				
$\overline{SW3} * SW2$				
$SW3 * SW2$				
$SW3 * \overline{SW2}$				

- If we can fill in these table values, we can figure out the circuit's behaviour.

# Segment 0 truth table

SW3	SW2	SW1	SW0	HEX[0]
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

# Segment 0 Karnaugh Map

- Now to fill in the table below....

	$\overline{SW1} * \overline{SW0}$	$\overline{SW1} * SW0$	$SW1 * SW0$	$SW1 * \overline{SW0}$
$\overline{SW3} * \overline{SW2}$	1	0	1	1
$\overline{SW3} * SW2$	0	1	1	1
$SW3 * SW2$	1	0	1	1
$SW3 * \overline{SW2}$	1	1	0	1

- What are the groupings that you see here?
  - Yes, overlapping is allowed 😊

# Segment 0 Karnaugh Map

- What are the equations for these groups?

	$\overline{SW1} * \overline{SW0}$	$\overline{SW1} * SW0$	$SW1 * SW0$	$SW1 * \overline{SW0}$
$\overline{SW3} * \overline{SW2}$	1	0	1	1
$\overline{SW3} * SW2$	0	1	1	1
$SW3 * SW2$	1	0	1	1
$SW3 * \overline{SW2}$	1	1	0	1

$$SW2 * SW1 * SW0$$

$$SW2 * SW1$$

$$SW3 * SW1 * SW0$$

$$SW3 * SW1$$


$$SW2 * SW1 * SW0$$

$$SW3 * SW0$$


Can you figure out which terms are inverted to make these groups work?
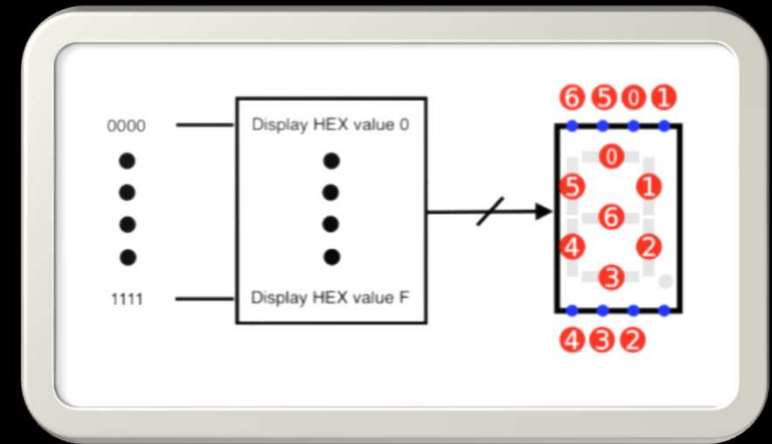
# Tasks for Lab 2

- Repeat this process seven times to implement the behaviour for each of the seven segments in the HEX display.
  - Try to get the minimal circuit for each!
- Once you're done, your seven circuits go into the decoder module in the middle of the diagram above.
  - Make sure to test each segment as you go!




# Using Logisim with DE1-SOC

 


 
# How 7-segments work on DE1


- The default for 7-segments on the **DE1** boards are “**active low**”, meaning that they turn on when their input signal is 0, not 1.
  - If you set segment 0 high, there is no voltage drop across the segment, so it doesn't turn on.
  - If you set segment 0 low, the voltage drop across the segment makes current flow, causing it to turn on.
- The default for 7-segments in **Logisim** are “**active high**” therefore you need to change this in properties.



# Activating 7-seg displays

- Need to set segment 0 (top segment) **low** in these input cases instead:

0000	--	"0"
0010	--	"2"
0011	--	"3"
0101	--	"5"
0110	--	"6"
0111	--	"7"
1000	--	"8"
1001	--	"9"
1010	--	"A"
1100	--	"C"
1110	--	"E"
1111	--	"F"

 

- How do we express this?


# Activating HEX displays

- Could also set segment 0 (top segment) **high** in the other input cases:

- 0001 -- "1"
- 0100 -- "4"
- 1011 -- "B"
- 1101 -- "D"

- Can be expressed as a four-part Boolean expression:

```
HEX[0] = ~SW[3] & ~SW[2] & ~SW[1] & SW[0] |  
          ~SW[3] & SW[2] & ~SW[1] & ~SW[0] |  
          SW[3] & ~SW[2] & SW[1] & SW[0] |  
          SW[3] & SW[2] & ~SW[1] & SW[0];
```

 

# Activating HEX displays

```
HEX[0] = ~SW[3] & ~SW[2] & ~SW[1] & SW[0] |  
         ~SW[3] & SW[2] & ~SW[1] & ~SW[0] |  
         SW[3] & ~SW[2] & SW[1] & SW[0] |  
         SW[3] & SW[2] & ~SW[1] & SW[0];
```

- Can this be reduced any further?
  - ...sadly, no ☹
- How do we know?
  - Karnaugh maps!

# Activating HEX displays

- Can you write the expressions for HEX[1] to HEX[6]?
- Can you reduce these expressions to the simplest gate form?

